
 


Properties & definitions of Digital ICs

 

Basic logic operations



Gate: A circuit performs a logic function.

Combinational Gates:
Logic Gates performs one or more of Basic operations.

Positive voltage logic

binary 0
(Low voltage)

binary 1
(High voltage)

Inverter:



Non-Inverter (Buffer)

Regenerate voltage levels

- * Making degraded high levels higher
- * " " low " lower





Ideal Logic elements

$$\text{Ideal } I_{CC} = 0$$

$$P_{CC} = I_{CC} V_{CC}$$

$$\text{Ideal } P_{CC} = 0$$

Typically 5V $\rightarrow V_{CC}$

  

Voltage transfer
characteristics
(VTC)

input 0:


voltage range $0 \leq V_{IN} < V_{CC}/2$

input 1:

voltage range $V_{CC}/2 < V_{IN} \leq V_{CC}$




$V_{IN} = V_{CC}/2$ has undefined output
& will cause unpredictable results
and is therefore avoided

Ideal Transient Characteristics

 

Ideal Input & Output gate impedances

   
Model of input & output impedance of a logic inverter



* The driving gate must provide enough output current to drive all the load gates

$$I_{out} = N I'_{IN}$$

 * Ideally an infinite input resistance is desired giving infinite driving capability.



* Faster switching time suggesting an ideal zero output resistance

* Smaller input capacitance will speed up switching time

* Infinite input resistance provide higher charging current for input capacitance

Inverter voltage transfer characteristic (VTC)

A most

$$V_{OH} > V_{IH}$$

and


$$V_{IL} > V_{OL}$$

For design we use worst case values of:

$$V_{OH}, V_{OL}, V_{IH}, V_{IL}$$

V_M : Midpoint voltage

V_{th} : threshold voltage

 


Inverter VTC

V_M is the point on VTC where $V_{out} = V_{in}$

 Example 1.1 Voltage Transfer Characteristic Critical Points

What are the critical voltages V_{OH} , V_{OL} , V_{IL} , V_{IH} , and V_M for the voltage transfer characteristic of Figure



Solution:

$$V_{OH} = 4.3V \quad V_{OL} = 0.2V$$

$$V_{IH} = 0.9V \quad V_{IL} = 0.7V$$

$$V_M = 0.9V$$

Logic swing & transition width

LS is the magnitude difference between the output high & low voltage levels


$$V_{LS} = V_{OH} - V_{OL}$$

TW is the amount of voltage change that is required of the input voltage to cause a change in the output voltage from high to low or vice-versa.

$$V_{TW} = V_{IH} - V_{IL}$$

 Example 1.2 Logic Swing and Transition Width

Determine the logic swing and transition width for the VTC of Figure



Noise in digital circuits

Noise is variations in steady state voltage levels of digital circuits

* Noise AKA voltage level degradation

Noise Margin

* The voltage noise margins represent a safety margin for the high & low voltage levels.

$$V_{NMH} = V_{OH} - V_{IH}$$

$$V_{NML} = V_{IL} - V_{OL}$$

* V_{NMH} & V_{NML} must be positive.

Noise Sensitivities

* The effects of input variations (on the output)

$$V_{NSH} = V_{OH} - V_M$$

$$V_{NSL} = V_M - V_{OL}$$

Noise Immunities


* The quantity noise immunity is the ability of a gate to reject noise

$$V_{NIH} = \frac{V_{NSH}}{V_{LS}}$$

$$V_{NIL} = \frac{V_{NSL}}{V_{LS}}$$

 Example 1.3 Noise Margins, Noise Sensitivities and Noise Immunities

Determine the noise margins, noise sensitivities, and noise immunities for the VTC displayed in Figure



Fan-In & Fan-Out

Fan-In The number of the inputs of a gate

Fan-out The n \approx n outputs of a gate.


$$N_{high} = \frac{I_{out}(high)}{I_{in}(high)}$$

$$N_{low} = \frac{I_{out}(low)}{I_{in}(low)}$$

$$N_{out} = \min(N_{low}, N_{high})$$

 Example 1.4 Maximum Fan-Out

The inverter of Figure 1.7 has the terminal currents $I_{IN}(\text{low}) = 2.43 \text{ mA (out)}$, $I_{IN}(\text{high}) = 98.9 \mu\text{A (in)}$, $I_{OUT}(\text{low}) = 54.3 \text{ mA (in)}$, and $I_{OUT}(\text{high}) = 71.4 \text{ mA (out)}$. What is the maximum fan-out?




Transient characteristics

- * Switching voltages from high to low or low to high requires a finite amount of time.
- * Propagation delay is the time delay between the change in input voltage & the output voltage response.
- * BJT's requires time to store & remove charge from base region.
- * The transient characteristics of digital circuits employing MOSFET's are limited by the gate oxide capacitance.

Switching Speed definitions

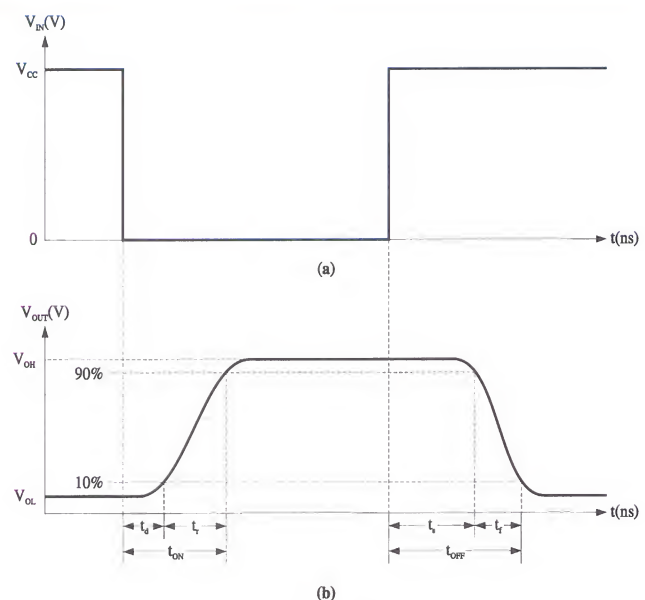- * $t_d \equiv$ delay time
- * $t_r \equiv$ rise time
- * $t_s \equiv$ storage time
- * $t_f \equiv$ fall time
- * $t_{on} \equiv$ turn on time $= t_d + t_r$
- * $t_{off} \equiv$ turn off time $= t_s + t_f$
- * t_r & t_f are the times associated with charging & discharging load capacitance.
- * t_d & t_s are associated with stored charge of PN junctions



Switching Speed Definitions: (a) Input pulse, (b) Output pulse



Propagations Delays

* The 50% points are used to define the time required for the output to respond to the input.

* $t_{PLH} \equiv$ the low to high propagation delay time

* $t_{PHL} \equiv$ the high to low propagation delay time

$$* t_{p(avg)} = \frac{t_{PLH} + t_{PHL}}{2}$$

  

Example 1.5 Transient Characteristics



For the input and output waveforms of Figure determine

(a) the switching times t_r and t_f

  (b) the propagation delay times t_{PLH} and t_{PHL} .

$$t_r \approx t_f \approx 168 ns$$

$$t_{PHL} \approx 100 ns \quad t_{PLH} \approx 250 ns$$




Power Dissipation

$$P_{CC}(OH)$$

$$P_{CC}(OL)$$


$$P_{CC}(avg) = \frac{P_{CC}(OH) + P_{CC}(OL)}{2}$$
 
$$P_{CC}(avg) = \left(\frac{I_{CC}(OH) + I_{CC}(OL)}{2} \right) V_{CC}$$



$$P_{Diss}(avg) = P_{CC}(avg) + P_{EE}(avg)$$
 
$$= \left(\frac{I_{CC}(OH) + I_{CC}(OL)}{2} \right) V_{CC} + \left(\frac{I_{EE}(OH) + I_{EE}(OL)}{2} \right) V_{EE}$$



$$P_{CC} = I_{CC} V_{CC}$$

$$P_{EE} = I_{EE} V_{EE}$$

$$P_{CC} = I_{CC} V_{CC} \quad , \quad P_{EE} = I_{EE} V_{EE}$$

Note: P_{EE} = positive power dissipation

Example 1.6 Average Power Dissipation

Determine the average power dissipation for a gate supplied by a 5 V power supply with $I(OH) = 1$ mA and $I(OL) = 3.18$ mA.

Power-delay products.

* Low power dissipation and short propagation delay times are both desirable for digital logic circuits.

* Faster propagation delay times are achieved at the cost of increased power dissipation.

* $P_{\text{diss}}(\text{avg}) \propto \frac{1}{t_p(\text{avg})}$

* power-delay product: $PD = P_{\text{diss}}(\text{avg}) t_p(\text{avg})$

* power-delay product \equiv speed-power product

* For Ideal gate $PD = 0$

Example 1.7 Power-Delay Product

The gate of example 1.6 has propagation delay times of $t_{\text{PHL}} = 1.4 \text{ ns}$ and $t_{\text{PLH}} = 3.2 \text{ ns}$. Calculate the power-delay product for this gate.